

- 1) The internal resistances of an ideal voltmeter and an ideal ammeter are respectively (ideal meaning the behavior of the system is not changed when using the meter)
  - a. zero and zero.
  - b. infinite and infinite.
  - c. zero and infinite.
  - d. **infinite and zero**
  
- 2) Three resistors, each with resistance  $R_1$ , are in series in a circuit. They are replaced by one equivalent resistor,  $R$ . Comparing this resistor to the first resistor of the initial circuit, which of the following is true?
  - a. **The current through  $R$  equals the current through  $R_1$ .**
  - b. The voltage across  $R$  equals the voltage across  $R_1$ .
  - c. The power given off by  $R$  equals the power given off by  $R_1$ .
  - d.  $R$  is less than  $R_1$ .
  
- 3) If  $R_1 < R_2 < R_3$ , and if these resistors are connected in series in a circuit, which one dissipates the greatest power?
  - a.  $R_1$
  - b.  $R_2$
  - c.  **$R_3$**
  - d. All are equal in power dissipation
  
- 4) Three resistors, each with resistance  $R_1$ , are in parallel in a circuit. They are replaced by one equivalent resistor,  $R$ . Compare this resistor to the first resistor of the initial circuit. Which of the following statements is true?
  - a. The current through  $R$  equals the current through  $R_1$ .
  - b. **The voltage across  $R$  equals the voltage across  $R_1$ .**
  - c. The power given off by  $R$  equals the power given off by  $R_1$ .
  - d.  $R$  is greater than  $R_1$ .
  
- 5) Three resistors, each of different value, are used in a circuit with a power source supplying 12 volts. For which of the following resistor combinations is the total power supplied the greatest?
  - a. all three resistors in series
  - b. **all three resistors in parallel**
  - c. two of the resistors in parallel with the third resistor in series with the parallel pair
  - d. This cannot be found until it is known which resistor is in series with the parallel pair.
  
- 6) Kirchhoff's rules are the junction rule and the loop rule. Which of the following statements is true?
  - a. Both rules are based on the conservation of charge.
  - b. Both rules are based on the conservation of energy.
  - c. **The junction rule is based on the conservation of charge, and the loop rule is based on the conservation of energy.**
  - d. The junction rule is based on the conservation of energy, and the loop rule is based on the conservation of charge.